
Truth Table and Logic Gates A.B В A' B' AB A'B' A'B AB' A A \mathbf{B} В A+B C 0 0 0 0 0 0 0 0 0 1 1 1 0 0 0 0 0 1 1 0 1 0 0 0 1 0 0 0 1 0 0 1 0 1 1 0 0 1 0 0 1 0 0 1 1 1 1 1 1 1 0 0 1 0 0 1 0 1 1 0 0 NOT 1 0 AND OR 1 1 0 1 1 1 P AND PQ ⊦**P.Q'** AND

- **1.** XY+XY
- **2.** XZ+Y'Z
- **3.** X'Y'+XY
- 4. X+YZ'
- **5.** X'Y'+YZ'
- **6.** AB+BC+C'D
- 7. AB'C+C'D
- 8. ABC+AB'C
- **9.** XY'+Z
- **10.** A(B'+C)
- **11.** (X+Y)(X+Z')
- **12.** (X'+Y')(X+Y')(X'+Y)

- 13. X(Y'+Z)
- **14.** A(B'+C')
- **15.** (A+B+C')(A'+B'+C)
- 16. (X+Y)(X'+Y')
- **17.** (C+B)A
- 18.AB+A'
- 19.(AB+AC)'
- 20. AB+A
- **21.** (A+B)(A+C)
- **22.** (A+B)(A+C)
- 23. AB+AC
- **24.** (A+B')(A'+C)(B'+C)


- **25.**A'B'C'
- 26.A'B+C'
- 27.B+C'+A
- 28.AB+AC'+BC
- 29.A'BC
- 30.A'+B+C
- 31.AB'C
- 32.(AB+C')D'
- **33.**(BC)'+A'
- **34.** (P'+Q)(Q'+P)
- **35.**((P'+Q)(P+Q))'
- **36.** (P'+Q)'+(Q'+P)


- **37.** (P'+Q)(P+Q')(Q'+Q)
- 38. ((P'+Q')(Q'+P))'
- **39.** (P'+Q')(Q'+P')
- **40.** (P'+Q')+(Q'+P)
- 41.(P+Q)'(Q
- **42.** (P+Q)'(Q'+P)
- 43.(P+Q)(Q'+P)'
- **44.**P'+Q')(P+Q')(Q'+P')
- 45.(P'+Q)(Q'+P')'
- **46.** (P'+Q')(P'+Q')
- **47.** (P'+Q)'+(Q'+P)'
- **48.** (P'+Q)(Q'+P)'(Q'+Q)

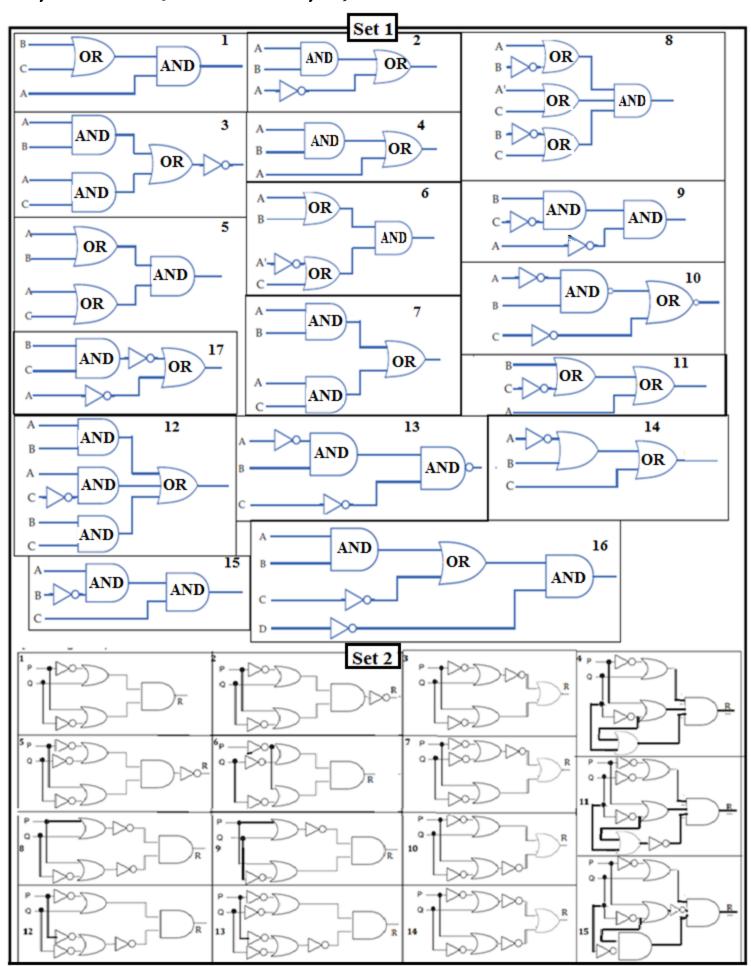

Page 2 | B-9, Bank Enclave, Shastri Nagar, Near KarteChowk Ghaziabadg9_sharma@yahoo.com


NOR => OR + NOT

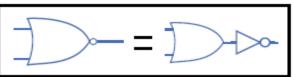

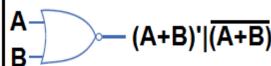


Change N=> C


NAND = AND + NOT

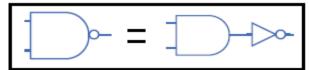




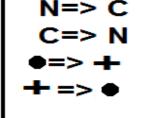


NAND+NAND=AND

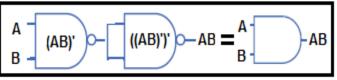


Example 1: YZ+XZ using NAND

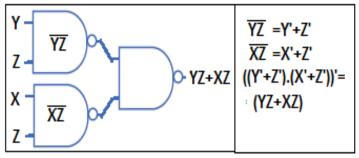


Example 2: X'Y+Y'Z using NAND

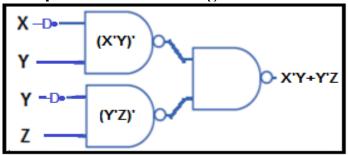


NOR+NOR=OR

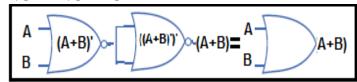

Example1: (X+Y)(Y+Z)(Z+X) using NOR

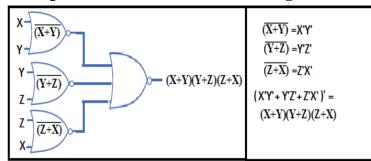

Example 2: (X'+Y)(Y'+Z)using NOR

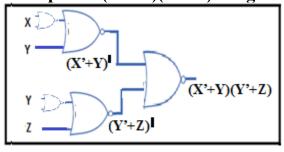


Using NAND:

- 1. XY+XY
- 2. XZ+Y'Z
- 3. X'Y'+XY
- 4. X+YZ'
- 5. X'Y'+YZ'
- 6. AB+BC+C'D
- 7. AB'C+C'D
- 8. ABC+AB'C'

Using NOR

- 1. XY'+Z
- 2. A(B'+C)
- 3. (X+Y)(X+Z')
- 4. (X'+Y')(X+Y')(X'+Y)
- 5. X(Y'+Z)
- 6. A(B'+C')
- 7. (A+B+C')(A'+B'+C)
- **8.** (X+Y)(X'+Y')

Conical Forms

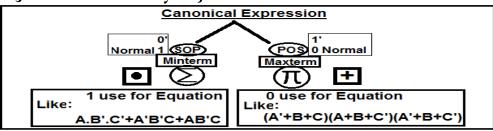

Example:


A	В	C	R	Position		SOP	POS
0	0	0	0	0	M0	A'B'C'	A+B+C
0	0	1	1	1	M1	A'B'C	A+B+C'
0	1	0	1	2	M2	A'BC'	A+B'+C
0	1	1	0	3	M3	A'BC	A+B'+C'
1	0	0	0	4	M4	AB'C'	A'+B+C
1	0	1	1	5	M5	AB'C	A'+B+C'
1	1	0	0	6	M6	ABC'	A'+B'+C
1	1	1	1	7	M7	ABC	A'+B'+C'

R=SOP=> A'B'C+A'BC'+AB'C+ABC OR R= $\sum \{1,2,5,7\}$


 $R=POS=>(A+B+C)(A+B'+C')(A'+B+C)(A'+B'+C) OR R=\pi\{0,3,4,6\}$


SOP				POS			
	Σ	0' & 1=>N		π	1' & 0=>N		
MO	000	A'B'C'	M0	0+0+0	A+B+C		
M1	001	A'B'C	M1	0+0+1	A+B+C'		
M2	010	A'BC'	M2	0+1+0	A+B'+C		
М3	011	A'BC	М3	0+1+1	A+B'+C'		
M4	100	AB'C'	M4	1+0+0	A'+B+C		
M5	101	AB'C	M5	1+0+1	A'+B+C'		
M6	110	ABC'	M6	1+1+0	A'+B'+C		
M7	111	ABC	M7	1+1+1	A'+B'+C'		

Direct sole using K-map

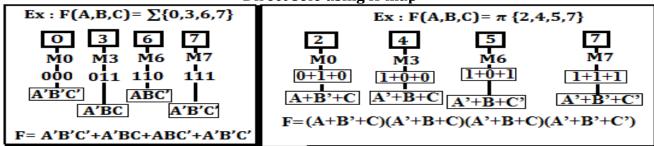

r Set 3										
D	Derive the SOP/ POS form of Boolean expression from the given truth table									
A	В	С	R 1	R 2	R 3	R 4	R 5	R 6	R 7	R8
0	0	0	0	0	0	0	0	1	1	0
0	0	1	1	1	1	1	0	1	1	0
0	1	0	1	0	0	1	1	1	1	0
0	1	1	1	1	1	1	1	1	0	0
1	0	0	1	1	0	1	0	0	0	1
1	0	1	0	0	1	1	0	0	0	1
1	1	0	0	0	0	0	1	1	0	1
1	1	1	1	1	1	1	0	1	1	1

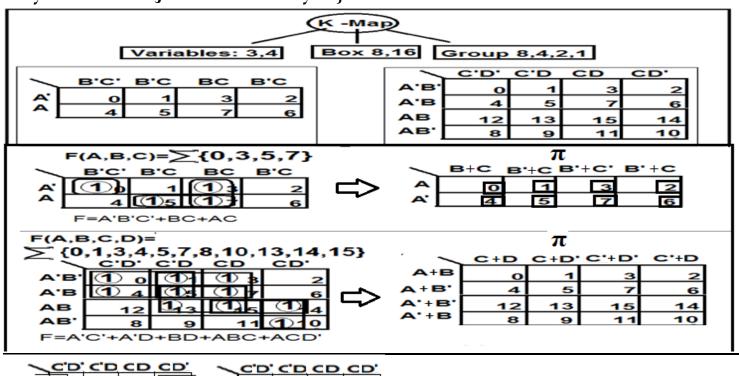

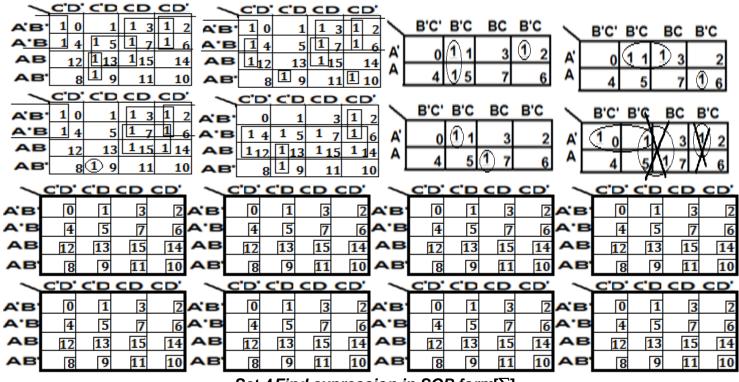

Set 4*Find expression in SOP form*[Σ]

- **1.** $F(a,b,c,d) = \sum \{0,1,3,4,5,7,8,9,11,12,13,15\}$
- **2.** $F(a,b,c,d) = \sum \{0,2,4,5,7,8,10,12,13,15\}$
- 3. $F(X,Y,Z,W_1) = \sum \{0,1,4,5,7,8,9,12,13,15\}$
- **4.** $F(W,X,Y,Z) = \sum \{0,2,7,8,10,15\}$
- **5.** $F(W,X,Y,Z) = \sum \{0,4,8,12\}$
- **6.** $F(W,X,Y,Z)=\Sigma\{2,3,6,10,11,14\}$

- 7. $F(A,B,C,D)=\Sigma\{0,1,3,4,5,6,7,9,10,11,13,15\}$
- **8.** $F(A,B,C,D)=\Sigma\{0,1,2,5,6,8,9,10,13,15\}$
- **9.** $F(X,Y,Z)=\Sigma \{3,4,5,6,7\}$
- **10.** $F(U,V,W,X)=\Sigma\{7,9,10,11,12,13,14,15\}$
- **11.** $F(W,X,Y,Z)=\Sigma\{2,3,6,10,11,14\}$
- **12.** $F(W,X,Y,Z) = \sum \{0,1,2,36,7,9,10,11,12,13,14\}$

Set 5Find expression in POS form[∏]

 $F(x, y, z, w) = \prod \{1,3,4,5,7,9,11,12,13,15\}$


 $F(x, y, z, w) = \prod \{2,6,8,10,14\}$


 $F(A,B,C,D)=\Pi\{0,1,3,4,5,6,7,9,10,11,13,15\}$

 $F(X,Y,Z)=\Pi\{3,4,5,6,7,14,15\}$

 $F(U,V,W,X)=\Pi\{0,2,3,7,8,10,11\}$

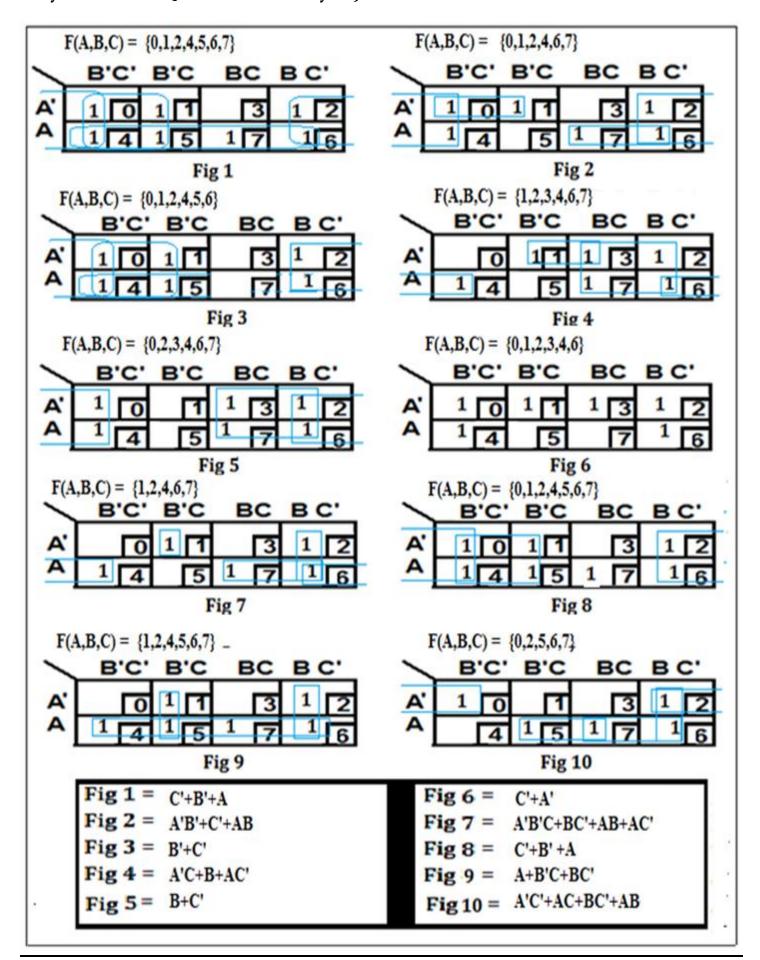 $F(U,V,W,X)=\Pi\{3,4,5,6,7,9,11,12,13,14,15\}$



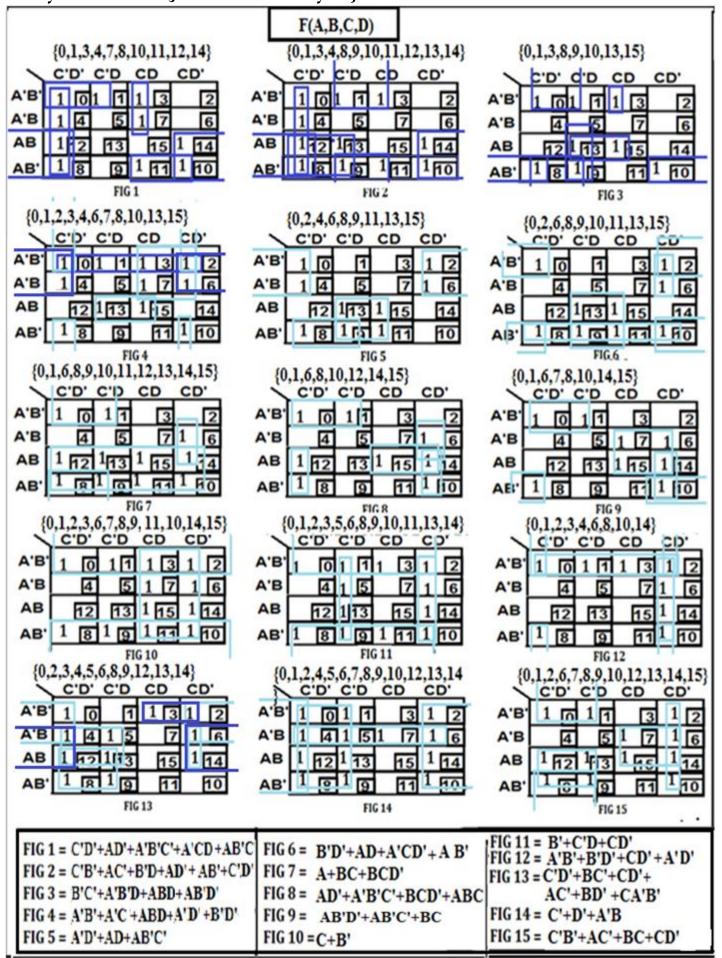

Set 1 Logic Gates

1. (C+B)A	7. AB+AC	13. AB'C
2. AB+A'	8. (A+B')(A'+C)(B'+C)	14. A'+B+C
3. (AB+AC)'	9. A'BC'	15. AB'C
4. AB+A	10. ((A'B)'+C')'	16. (AB+C')D'
5. (A+B)(A+C)	11. B+C'+A	17. (BC)'+A'

6. (A+B)(A+C)**12.** AB+AC'+BC

Set 2 Logic Gates

6. (P'+Q')(Q'+P')1. (P'+Q)(Q'+P)11.P'+Q')(P+Q')(Q'+P') 2. ((P'+Q)(P+Q))' 7. (P'+Q')+(Q'+P)12.(P'+Q)(Q'+P')' 3. (P'+Q)'+(Q'+P)8. (P+Q)'(Q'+P)' 13.(P'+Q')(P'+Q') 4. (P'+Q)(P+Q')(Q'+Q)9. (P+Q)'(Q'+P) 14.(P'+Q)'+(Q'+P)'

5. ((P'+Q')(Q'+P))' 10.(P+Q)(Q'+P)'15.(P'+Q)(Q'+P)'(Q'+Q)

Set 3 POS/SOP					
R1	SOP	A'B'C+A'BC'+A'BC+AB'C'+ABC			
	POS	(A+B+C)(A'+B+C')(A'+B'+C)			
R2	SOP	A'B'C+A'BC+AB'C'+ABC			
	POS	(A+B+C)(A+B+C)(A'+B+C')(A'+B'+C)			
R3	SOP	A'B'C+A'BC+AB'C+ABC			
	POS	(A+B+C)(A+B'+C)(A'+B+C)(A'+B'+C)			
F4	SOP	A'B'C+A'BC'+A'BC+AB'C'+AB'C+ABC			
	POS	(A+B+C)(A+B'+C)			
R5	SOP	A'BC'+A'BC+ABC'			
Ko	POS	(A+B+C)(A+B+C')(A'+B+C')(A'+B'+C')(A'+B+C)			
R6	SOP	A'B'C'+A'B'C+A'BC'+A'BC+ABC'+ABC			
KO	POS	(A'+B+C)(A'+B+C')			
R7	SOP	A'B'C'+A'B'C+A'BC'+ABC			
	POS	(A+B'+C')(A'+B+C)(A'+B+C')(A'+B'+C)			
R8	SOP	AB'C'+AB'C+ABC'+ABC			
	POS	(A+B+C)(A+B+C)(A+B'+C)(A+B'+C')			

